```
Prob_17.3.b.vhd 1/1
~/EE_316_Labs/Homework_10/ 05/02/2016
```

```
--Problem 17.3 (b)
-- REMARKS: The Counter_4 is carried over from part (a).--
entity Counter_8 is
 port(ClrN, LOAD, ENT, ENP, UP: std_logic; -- 1 bit inputs
    D: in std_logic_vector(7 downto 0);
     Q: out std_logic_vector(7 downto 0);
    Co: out std_logic);
end Counter_8;
architecture State_8 of Counter_8 is
 --- Counter_4 has parameters inside this declaration. Thus, the overloading
 --- of names does not matter (even though it is confusing).
 component Counter_4
   port (ClrN, LOAD, ENT, ENP, UP: std_logic; -- 1 bit inputs
        D: in std_logic_vector(3 downto 0);
        Q: out std_logic_vector(3 downto 0);
        Co: out std_logic);
 end component;
 signal ic: std_logic; -- "internal conversion"
 begin
   Q_Right: Counter_4 port map (ClrN, LOAD, ENT, ENP, UP,
                                                                -- inputs
                                D(3 downto 0), Q(3 downto 0), ic); -- outputs
   Q_Left: Counter_4 port map (ClrN, LOAD, ic, ENP, UP,
                               D(7 downto 4), Q(7 downto 4), Co);
end State_8;
```