

```
-----  
--Problem 17.4--  
-----
```

```
entity 4_to_1_Mux is  
  port (A, B, C, D: in std_logic;  
        Z: out std_logic);  
  
end 4_to_1_Mux;  
  
architecture out_z of 4_to_1_Mux is  
  signal I: std_logic_vector(1 to 0);  
  
begin  
  I <= A & B;  
  
  process (A,B,C,D)  
    case I is  
      when "00" =>  
        Z <= (not C) or D;  
      when "01" =>  
        Z <= C;  
      when "10" =>  
        Z <= (not C) xor D;  
      when "11" =>  
        Z <= (not D);  
    end case;  
  end process;  
end out_z;
```